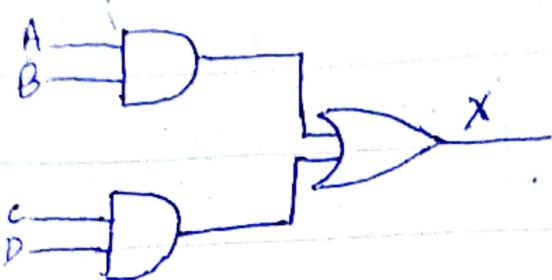


Chapter: 05

Ex: 5.1


① AND-OR LOGIC:



$$(AB) + (CD)$$

$$\cancel{(A+B)(C+D)}$$

② AND-OR-INVERT LOGIC:

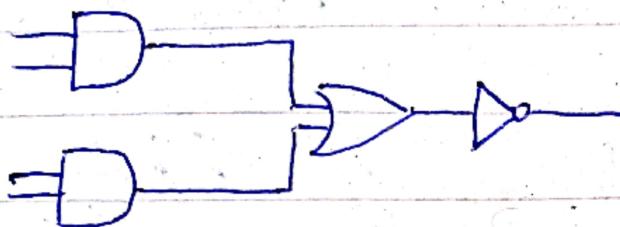


$$\overline{AB} + \overline{CD}$$


$$\overline{AB} \overline{CD}$$

$$(\overline{A}+\overline{B})(\overline{C}+\overline{D})$$

③ XOR logic

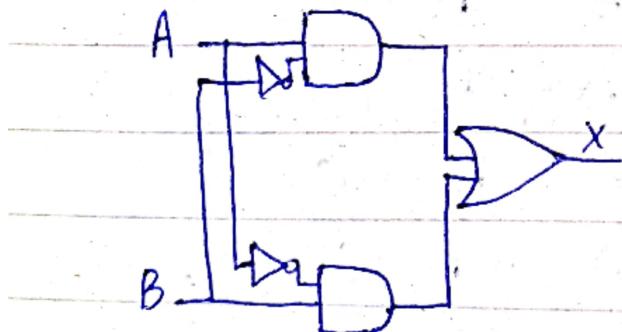

④ XNOR logic

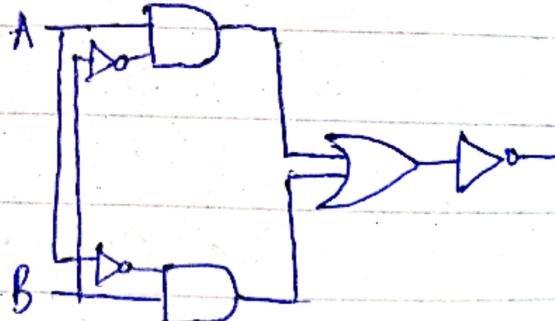

$$A\bar{B} + \bar{A}B$$

$$\overline{A}\bar{B} + \bar{A}B = (\overline{A}\bar{B})(\bar{A}B)$$

$$(\overline{A}+\bar{B})(\bar{A}+B) = (\overline{A}+B)(A+\bar{B})$$

$$= \overline{AA} + \overline{AB} + AB + B\bar{B}$$



5.1 Checkup:

$$1) A=1, B=0, C=1, D=0 \\ AB=0, CD=0, X=0 \rightarrow$$

$$2) A=1, B=1, C=0, D=1$$

$$AB=1, CD=0, X=1 \rightarrow \textcircled{0}$$

$$3) A=0, B=1, C=1, D=1$$


$$AB = 0, CD = 1, X = 1 \rightarrow \textcircled{0}$$

5.2 checkup

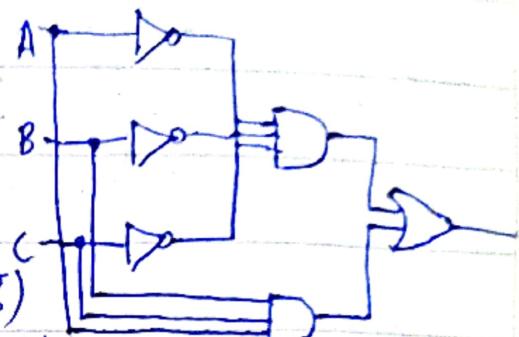1) EZ

$$2) \quad \begin{array}{ccc} 0 & 0 & 0 \\ 1 & 1 & 1 \end{array}$$

$$3) \quad ABC(D + \bar{D}) + AB(C + \bar{C})(D + \bar{D}) + AC(B + \bar{B})(D + \bar{D})$$



$$ABCD + ABC\bar{D} + ABCD + A\bar{B}CD + A\bar{B}C\bar{D} + AB\bar{C}\bar{D} + AB(CD) + A\bar{B}CD + AB\bar{C}\bar{D} + A\bar{B}C\bar{D}$$

	00	01	11	10
00	00			
01		01		
11	11	11	11	11
10	10	10	10	10



$$AB + AC \quad (\text{By K-Map})$$

5.3 Checkup:

$$a) X = \bar{A} + B$$

or

$$b) X = \overline{AB}$$

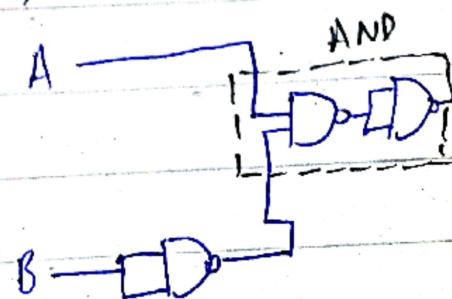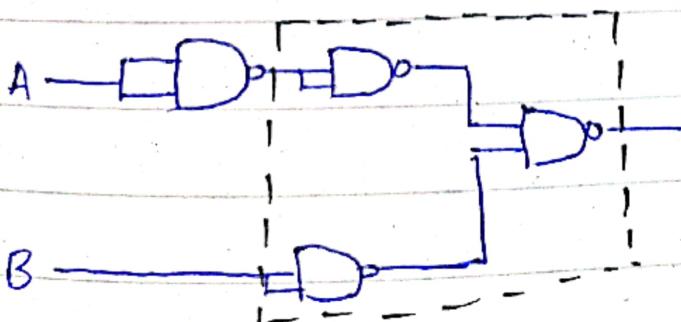

0	0	1	0	1	1
0	1	1	0	0	1
1	0	0	1	1	0
1	1	1	0	0	1

5.1 Checkup:

1) $A=1, B=0, C=1, D=0$

$$AB = 0, CD = 0, X = 0 \rightarrow \textcircled{1}$$

2) $A=1, B=1, C=0, D=1$

$$AB = 1, CD = 0, X = 1 \rightarrow \textcircled{2}$$

3) $A=0, B=1, C=1, D=1$

$$AB = 0, CD = 1, X = 1 \rightarrow \textcircled{3}$$

2) a) $A=1, B=0, C=1, D=1$

b) $A=1, B=1, C=0, D=1$

c) $A=0, B=1, C=1, D=1$

d) $A=0, B=0, C=1, D=0$


5.2 Checkup

1) EZ

2) $0 \quad 0 \quad 0 \quad 1 \quad A\bar{B}\bar{C}$

$1 \quad 1 \quad 1 \quad 1 \quad A\bar{B}C$

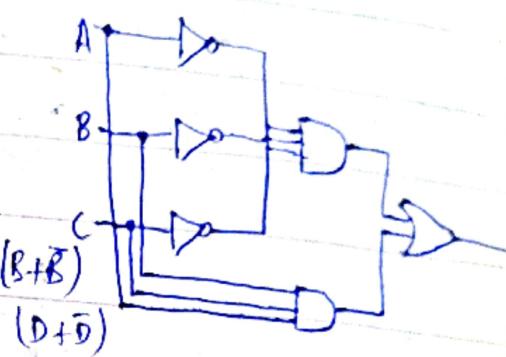3) $ABC(D+\bar{D}) + AB(C+\bar{C})(D+\bar{D}) + AC(B+\bar{B})(D+\bar{D})$



$$ABCD + ABC\bar{D} + ABCD + ABC\bar{D} + A\bar{B}C\bar{D} + A\bar{B}C\bar{D} + A\bar{B}CD + \bar{A}BC\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D}$$

$$+ A\bar{B}C\bar{D}$$

	00	01	11	10
00				
01				
11	1	1	1	
10			1	1



AB + AC (By K-Map)

5.3 Checkup:


a) $X = \bar{A} + B$

OR

b) $X = A\bar{B}$

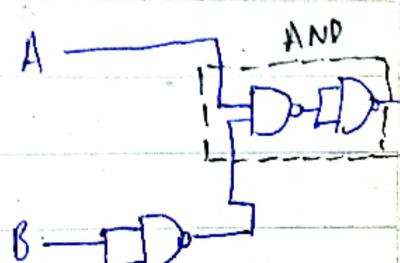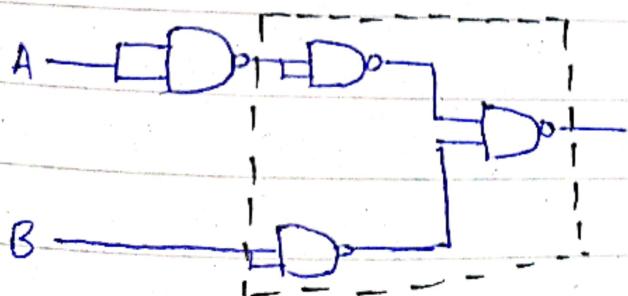

0	0	1	0	1	1
0	1	1	0	0	1
1	0	0	1	1	0
1	1	0	1	0	1

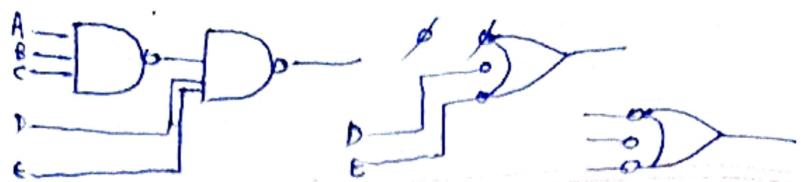


#Section 5.4

- $\text{NAND} = \text{Neg OR (De Morgan)}$



$$\overline{D} \rightarrow \overline{\overline{D}}$$

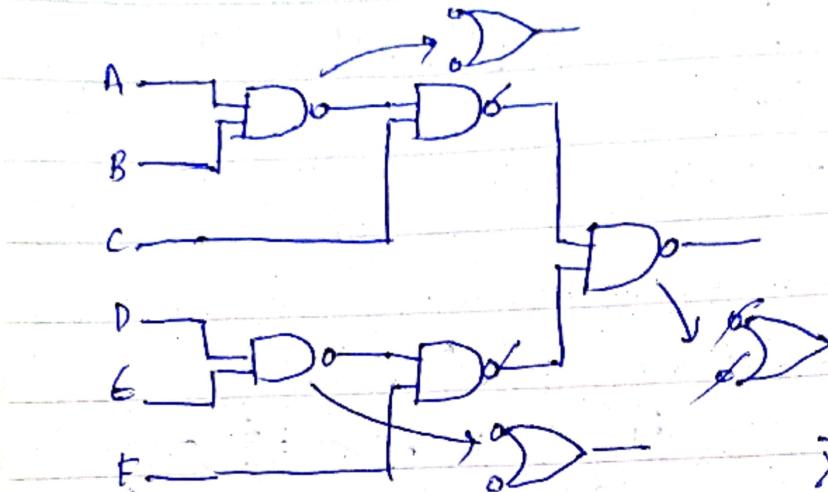- Bubble cancel out when NOT on both sides,



$$\overline{X+Y} = \overline{X}\overline{Y}$$
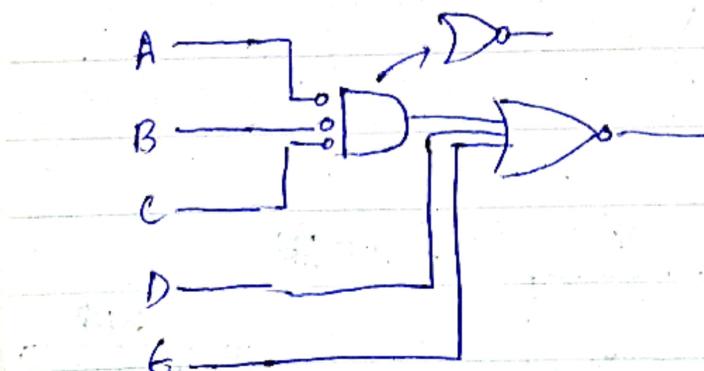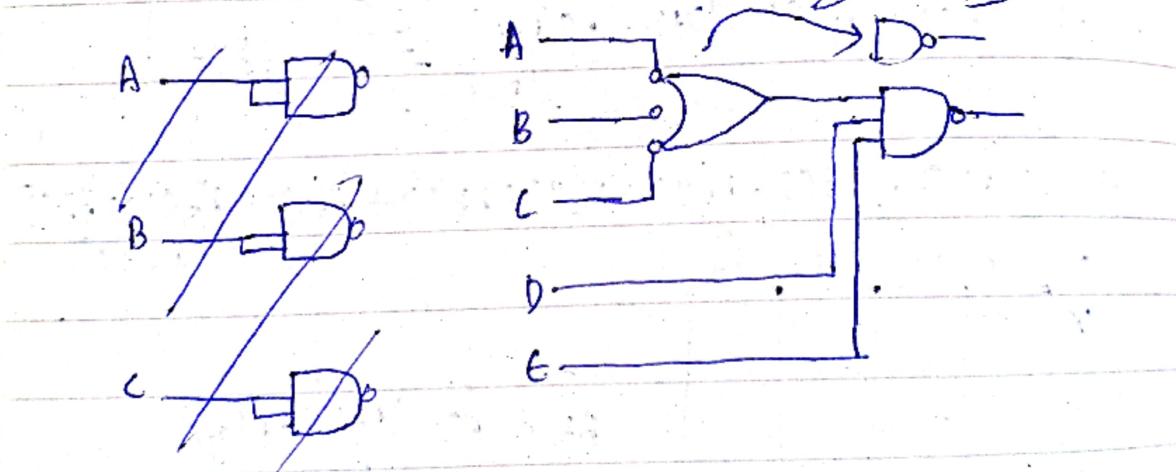
$$\overline{X} \rightarrow \overline{D}$$



Chapter : 06

* Half Adder

$$0 + 0 = 0$$

$$\cdot C_{\text{out}} = AB$$


$$0 + 1 = 1$$

generated only when 1
both (so AND gate)

$$1 + 0 = 1$$


$$1 + 1 = 0 \text{ carry } 1 \quad \cdot \Sigma = A \oplus B$$

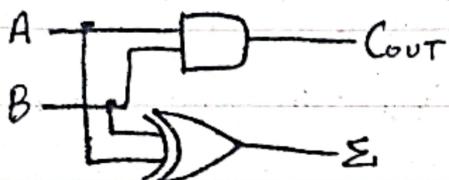generated 1 only when
different inputs (so XOR)



• Two inputs, 1 carry, 1 sum

* Full Adder:

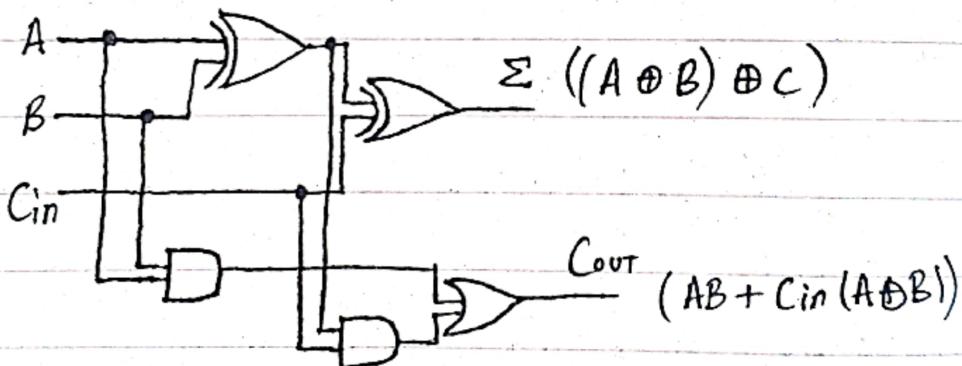

• 3 inputs, 1 carry, 1 sum

Example:

F.A = ? when A=1, B=1, Cin=1 ?

$$1 + 1 + 1 = 1 \text{ carry } 1$$

* SECTION 6.1:

a) 01

1 carry 0

b) 00

0 carry 0

c) 10

1 carry 0

d) 11

0 carry 1


\cdot 4 bit num = 4 FA
 \cdot 3 + " = 3 "

Num of bit = Num of FA

* Parallel Binary Adders:

- Cascade connection of full adders
- Need arise when we wanted to use adder for multibit 2 number as full adder can only comprehend 2 singlebit & 1 carry.

Example:

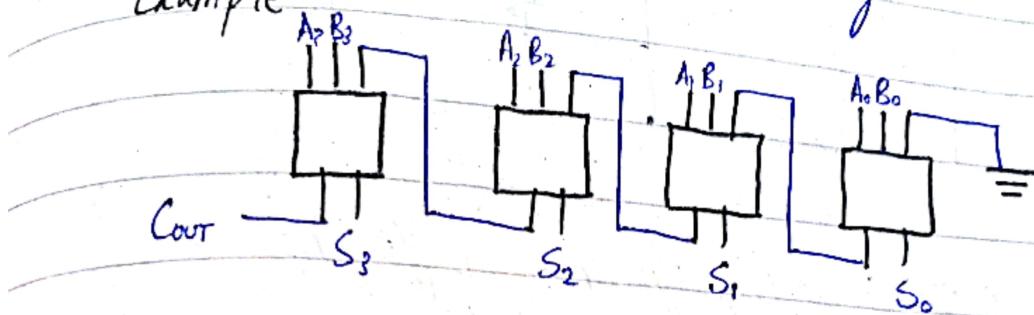


- 4 parallel full adders used for 4 bit 2 numbers

Example: 6.3


$$A = 1100$$

$$B = 1100$$

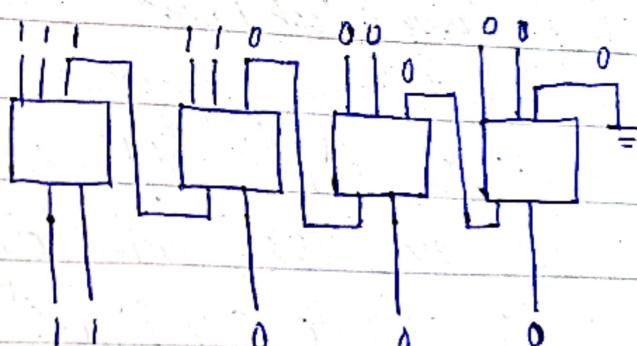


- Cout of 1 adder being input in higher order adder is called internal carries.

• 6.2 checkup:

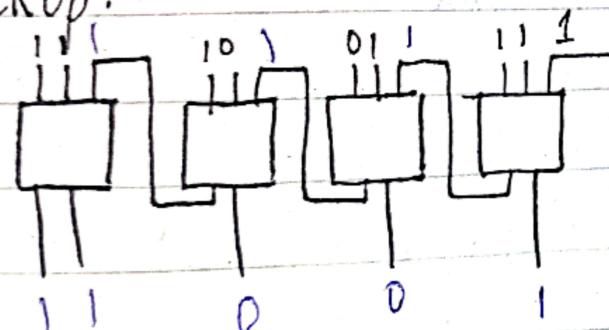

Related Problem

3 FA to implement 12 bit adder

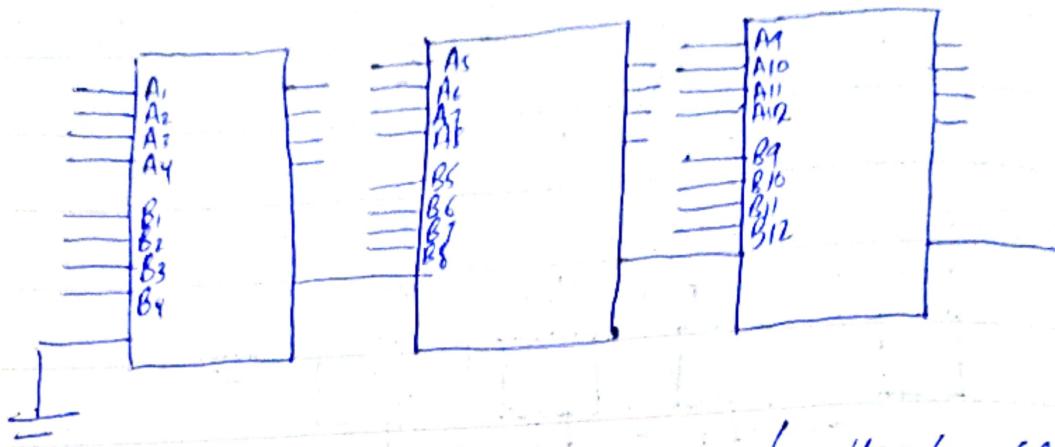

- Application is Voting system for yes/no see fig 6-13 in book

* Ripple Carry & look Ahead

- The delay in carry propagation from Cout of previous adder to Cin of next adder cause time delay
- In worst case, there is such delay in each adder making it quite significant in last adder output
- When no carry produced (best case) addition time = Propogation time

The concept of look ahead is predicting Cout without waiting for input from Cin.

- We predict Cout is 1 when ?

A	B	Cin	Cout
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

only 1 written
 $A \oplus B \& C_{in}=1 \rightarrow (A \oplus B) \cdot C_{in}$
 Carry
 Propagator (P)
 when AB both 1 $\rightarrow AB$
 Carry
 generator (G)

$$C_{out} = AB + (A \oplus B)C_{in}$$

$$= G + PC_{in}$$

by derivation of parallel look ahead adder, C_{out}
 dependant only on C_{in1} and $G_g \& C_p$

Exercise 6.3 Checkup:

$$1) A=1, B=0, C_g=? , C_p=?$$

$$\cdot C_g = AB \rightarrow (1)(0) = 0$$

$$\cdot C_p = (1) \oplus (0) = 1$$

$$2) C_{out} = ? \text{ when } C_{in}=1, C_g=0, C_p=1$$


$$C_{out} = (0) + (1)(1) = 1$$

* Comparator:


① Equality ($0 \rightarrow$ when diff, $1 \rightarrow$ when same)

• Use XNOR gate

for one bit two num, use XNOR gate

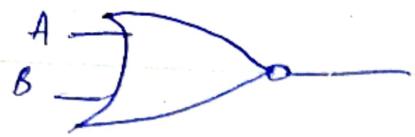


Two, 2 bit number

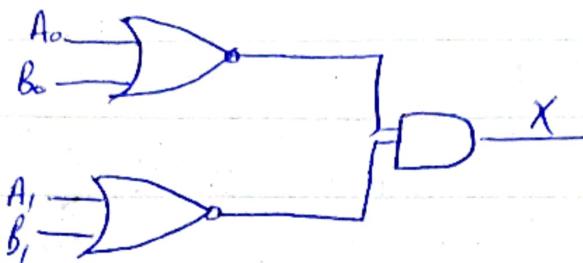


"1 when 1 from
both XOA XNOR,
1 from XNOR only
when same input"

Example: 6.5:

a) 10 and 10

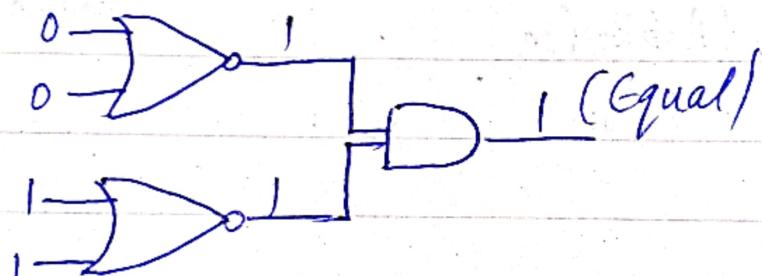

b) 11 & 10

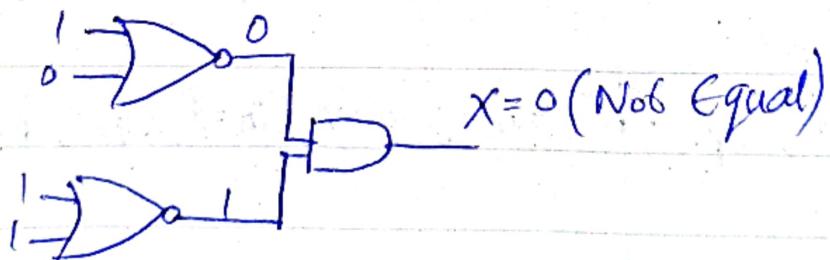


→ Inequality:


- Provide additional info $A > B$ or $A < B$
- Compare MSB A_3 and B_3

If different
 $A > B$ or $A < B$


If same, check
 $A_2 \neq B_2$

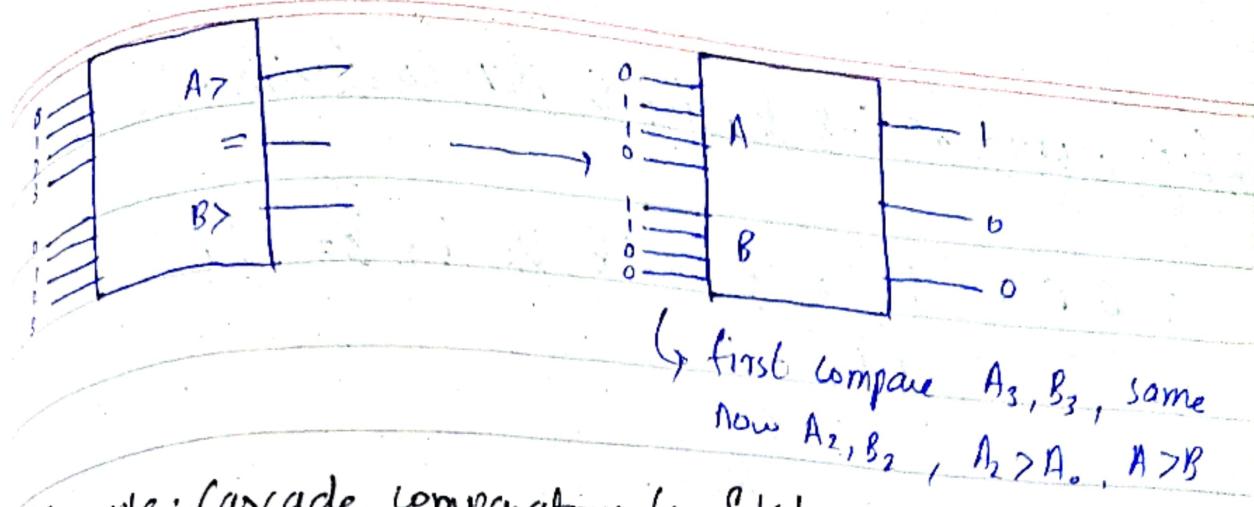

Example: Cascade comparators for 8 bit

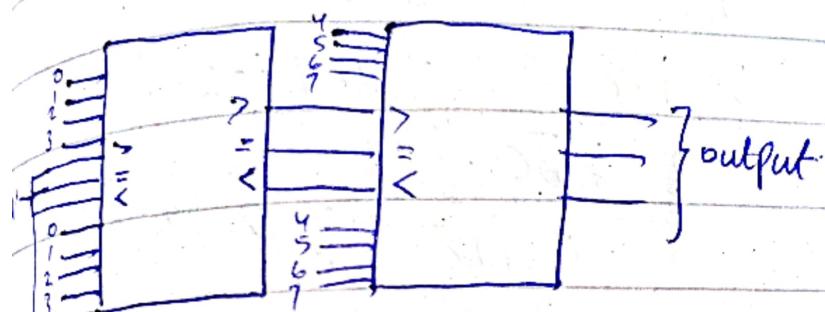


Decoders:

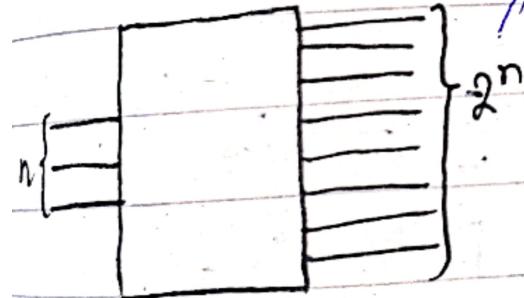

• 1 - 2 decoder, 2 - 4 decoder,
3 - 8 decoder, 4 - 16 decoder....


• In given conditions, only 1 output is high at a time

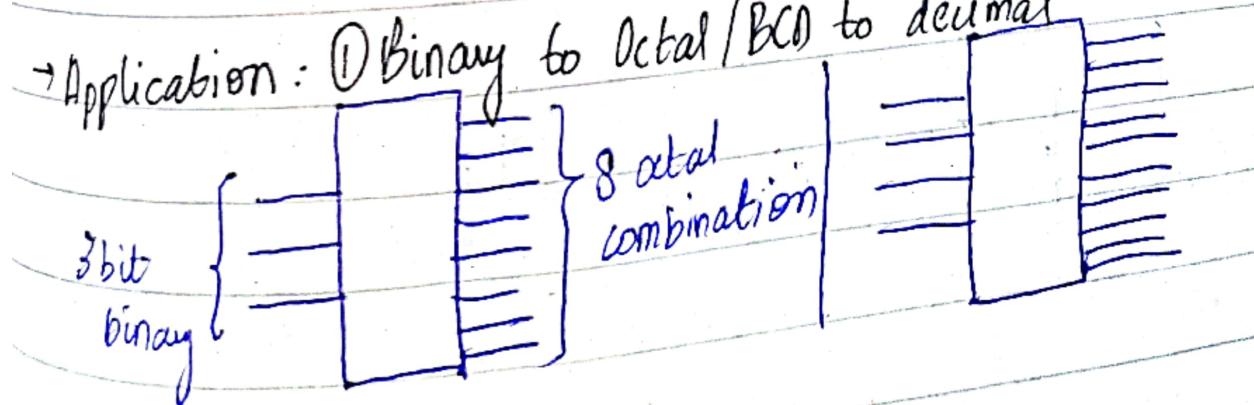→ Application: ① Binary to Octal / BCD to decimal



* Logic diagram of 3-8 decoder & BCD to decimal

A	B	C	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	D ₈	D ₉
0	0	0	$D = \bar{A}\bar{B}\bar{C}$									
0	0	1		$D = \bar{A}\bar{B}C$								
0	1	0		$D = \bar{A}BC$								
0	1	1		$D = \bar{A}BC$								∴ Active low
1	0	0		$D = A\bar{B}\bar{C}$								Use high active
1	0	1			$D = A\bar{B}C$							for 1 on appropriate
1	1	0				$D = ABC$						output
1	1	1					$D = A \cdot BC$					

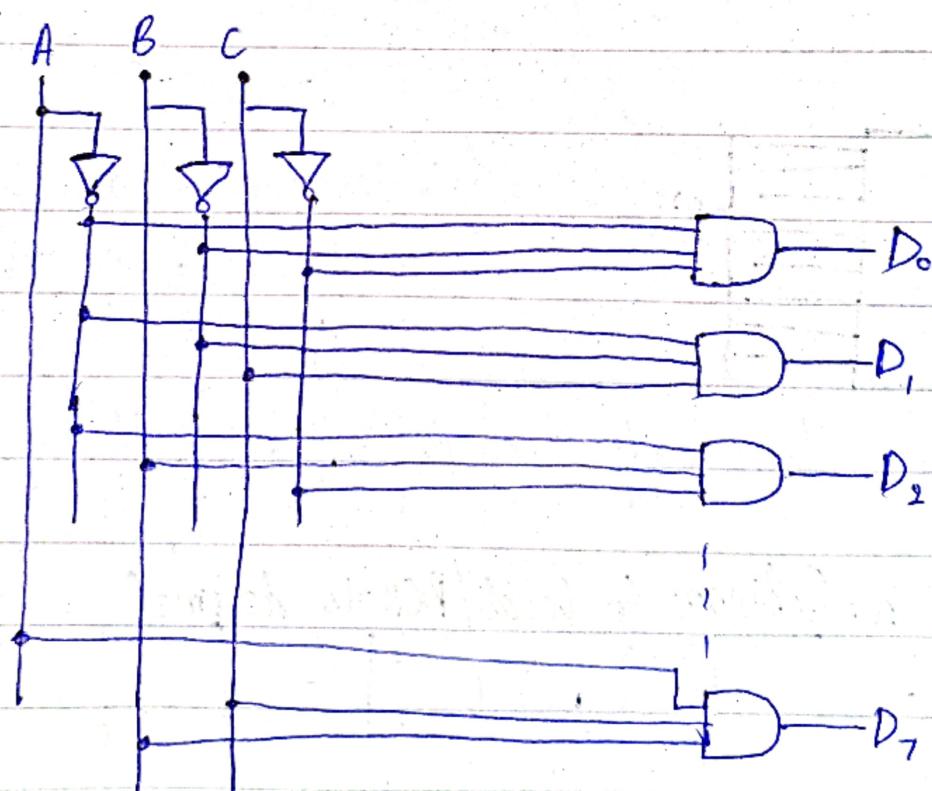

- Enable pin is also there but we assume it as high always

* BCD to decimal decoder

• Use 4-16 decoder (only 10 outputs as BCD is 0-9)

A B C D

0 0 0 0

0 0 0 1

0 0 1 0

0 0 1 1

0 1 0 0

0 1 0 1

0 1 1 0

0 1 1 1

1 0 0 0

1 0 0 1

1 0 1 0

1 0 1 1

1 1 0 0

1 1 0 1

1 1 1 0

1 1 1 1

D₁ D₂ D₃ D₄ D₅ D₆ D₇ D₈ D₉ D₁₀ D₁₁ D₁₂ D₁₃

$$D_1 = \bar{A}\bar{B}\bar{C}\bar{D}$$

$$I = \bar{A}\bar{B}\bar{C}\bar{D}$$

$$I = \bar{A}\bar{B}C\bar{D}$$

$$I = \bar{A}\bar{B}C\bar{D}$$

$$I = \bar{A}B\bar{C}\bar{D}$$

$$I = \bar{A}B\bar{C}\bar{D}$$

$$I = \bar{A}B\bar{C}\bar{D}$$

$$I = \bar{A}B\bar{C}\bar{D}$$

$$I = \bar{A}\bar{B}\bar{C}\bar{D}$$


$$I = \bar{A}\bar{B}\bar{C}\bar{D}$$

BCD not greater than 9

14/15/16


• For higher order decoder we will use multiple low order decoder to make it cost effective & less complex

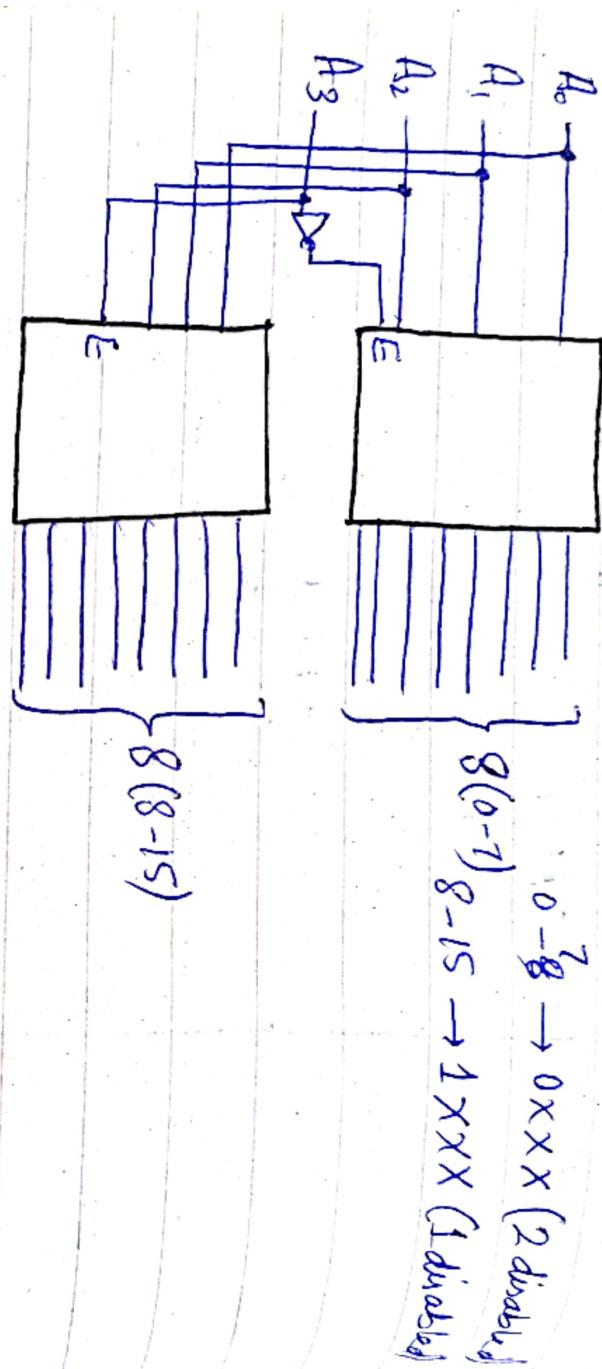* 4-16 decoder using 3-8 decoder
↳ 8 output, 16 needed, use 2 decoders



* 3-8 decoder using 2-4 decoder


↳ 4 output, 8 needed, 2 required

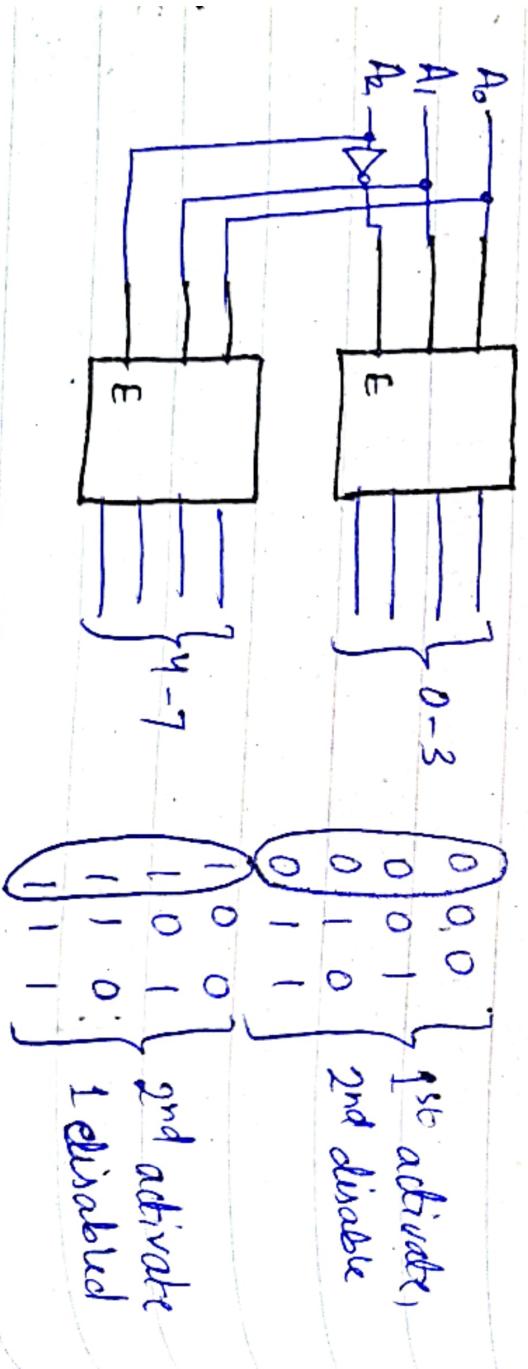

* 5-32 wiring 3-8 decoder

↳ 8 output, 4 decoders needed

A_0
 A_1
 A_2
 A_3

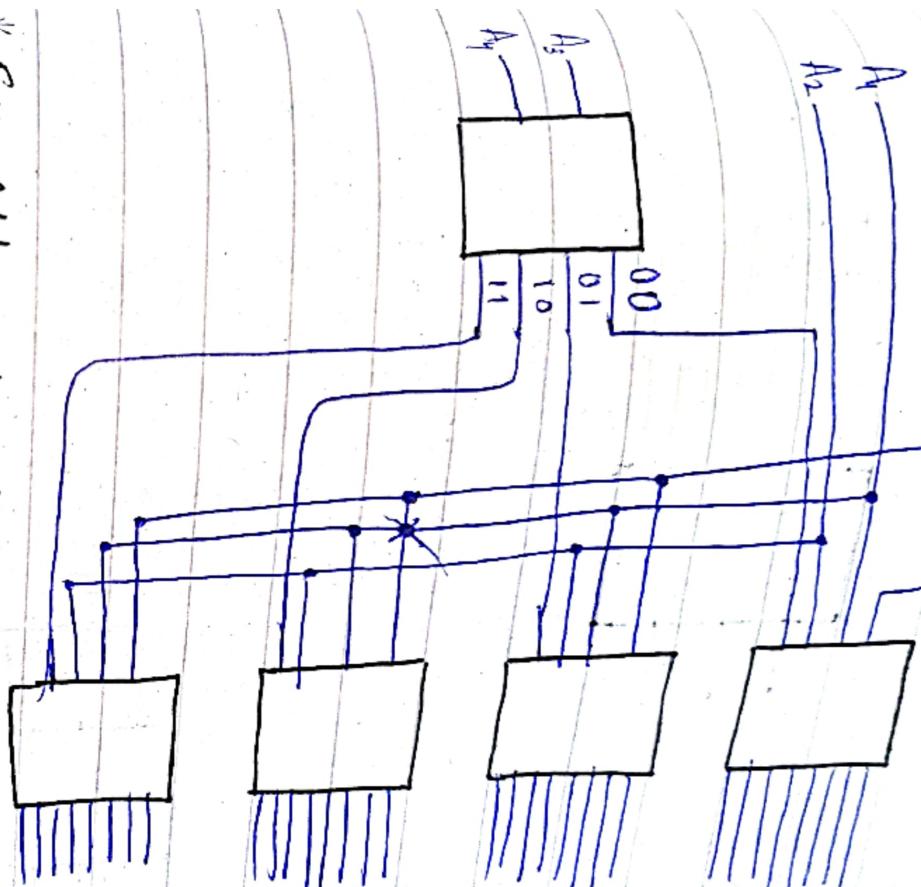

* Full Adder wiring decoder
 ↴


Use 3-8 decoder

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


* 3 bit even parity checker using decoder

A	B	C	P
0	0	0	0
0	0	1	1
0	1	0	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

i.e. 3-8 decoder

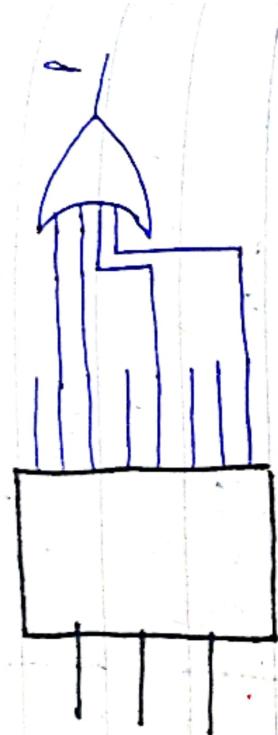


* Encoder

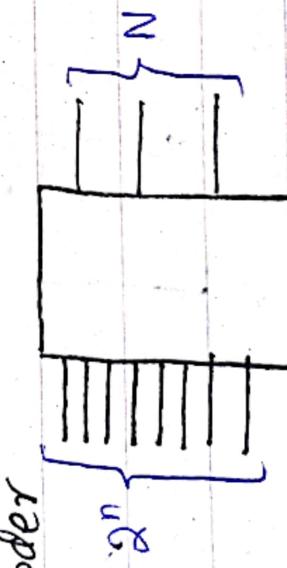

D₀ D₁ D₂ D₃ A B


1 1 1 1 0 0 i.e. 4-2 encoder

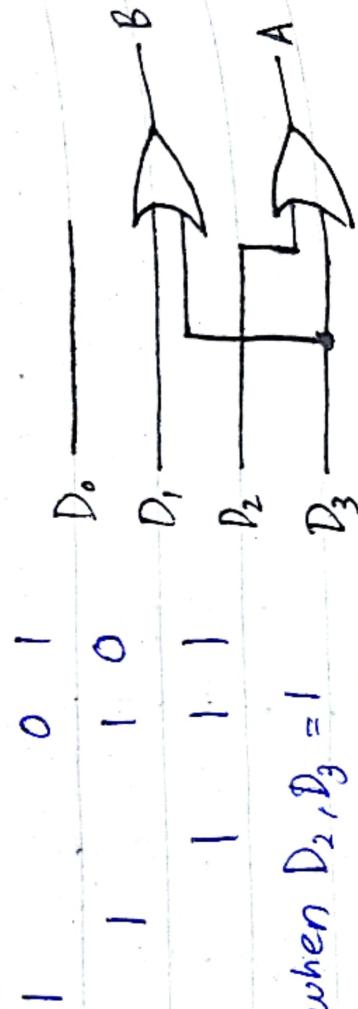

• A=1, when D₂, D₃=1

• B=1, when D₁, D₃=1

-8-3 line encoder

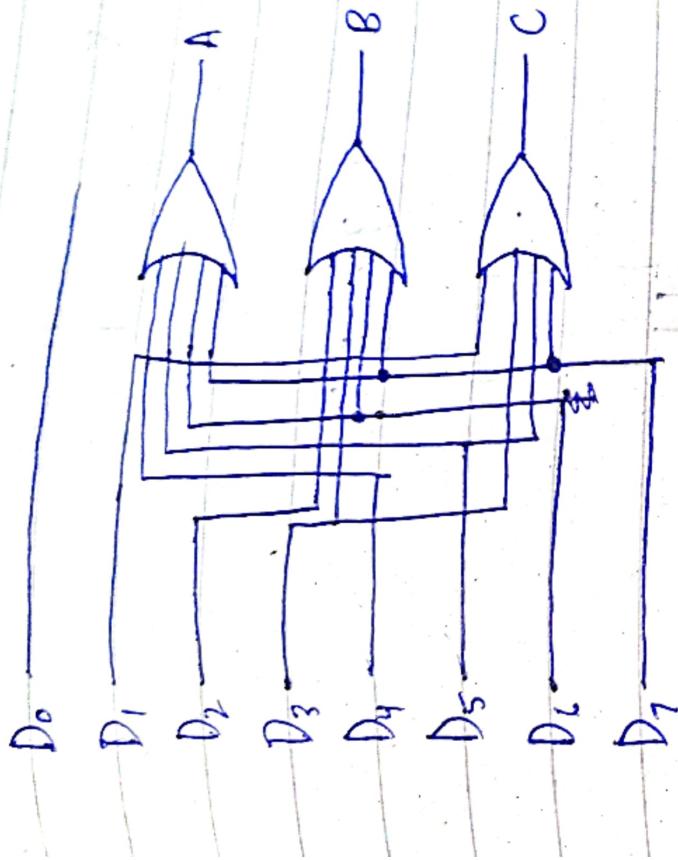


- limitation is D₀ is not connected to any and if D₂D₃ are high simultaneously it will make incorrect output for example "011" when D₄ & D₅ high simultaneously making D₃ as high, which is wrong.

- Now we use priority encoder, so input with higher subscript have higher priority
• In this case when D₁ & D₂ high simultaneously, D₂ will get priority making

→ Example 6.7 Check 6.6
If $I = 0010$, $q = 1001 \Rightarrow 1011$ (Not a valid BCD)

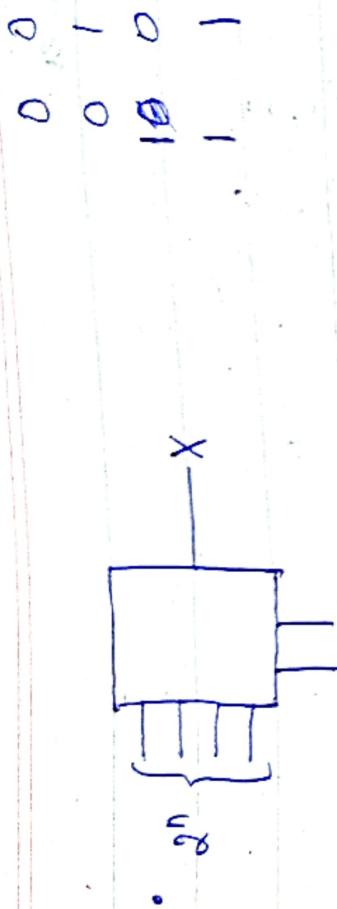- a) $I = 0010$, $q = 1001 \Rightarrow 1011$
- b) $I = 0001$, $q = 0101 \Rightarrow$



* 2x1 MUX

* 4x1 MUX



$S \quad Y$

$0 \quad D_0$

$1 \quad D_1$

$$Y = \bar{S}D_0 + SD_1$$

$0 \quad 0 \quad D_0$

$0 \quad 1 \quad D_1$

$1 \quad 0 \quad D_2$

$1 \quad 1 \quad D_3$

* 8x1 MUX

$S_2 \quad S_1 \quad S_0 \quad Y$

$0 \quad 0 \quad 0 \quad D_0$

$0 \quad 1 \quad 0 \quad D_1$

$0 \quad 1 \quad 1 \quad D_2$


$1 \quad 0 \quad 0 \quad D_3$

$1 \quad 0 \quad 1 \quad D_4$

$1 \quad 1 \quad 0 \quad D_5$

$1 \quad 1 \quad 1 \quad D_6$

$1 \quad 0 \quad 0 \quad D_7$

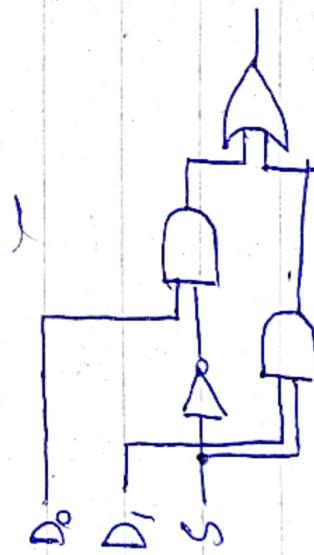

$Y = \bar{S}_2\bar{S}_1\bar{S}_0D_0 + \bar{S}_2\bar{S}_1S_0D_1 + \bar{S}_2S_1\bar{S}_0D_2 + \bar{S}_2S_1S_0D_3 + \dots + S_2S_1S_0D_7$

* Making 8x1 MUX using 4x1 MUX

