
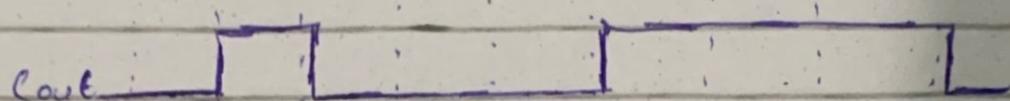
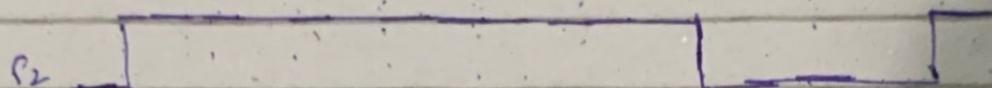


23/10/2021



Kirsh
Kumar

Date _____

Question 1

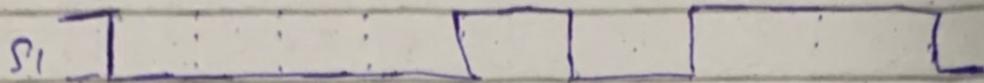

Q:2)

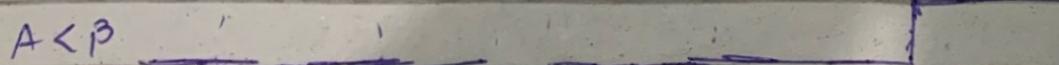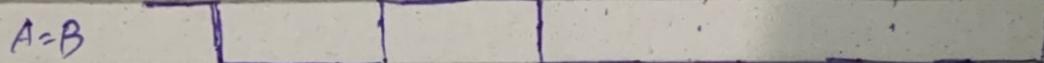


RC

No. _____


Date _____

Question.03


H01

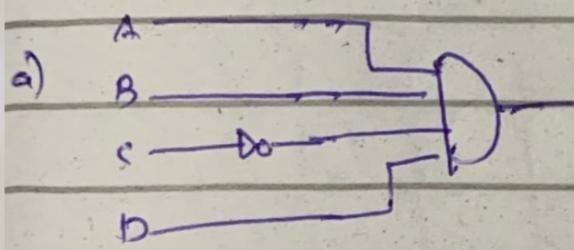


b) 1000

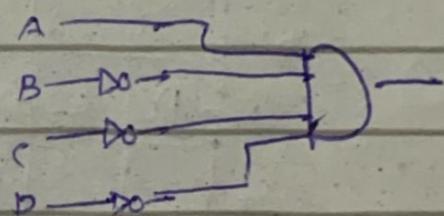

c) 11011

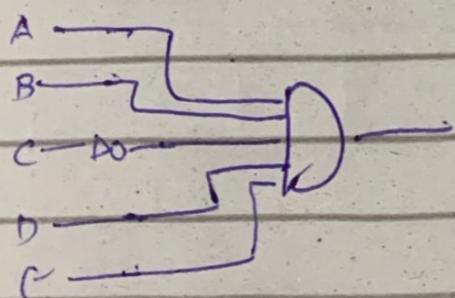


d) 11100

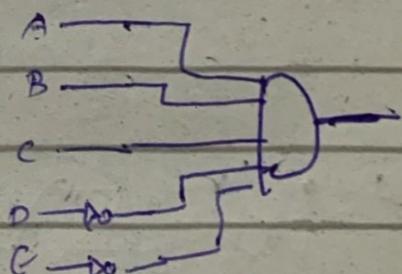


Q3

Date _____

Question: 04

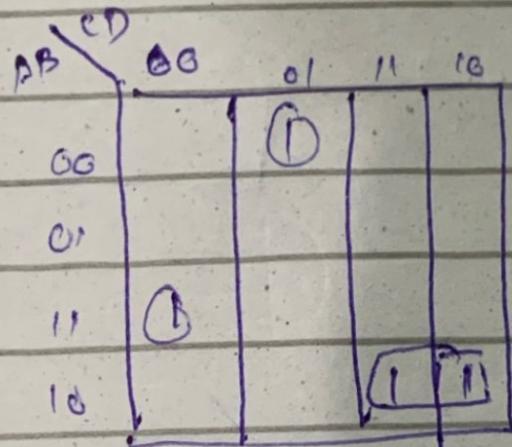

$$\bar{A}B\bar{C}D + AB\bar{C}\bar{D} + A\bar{B}C$$

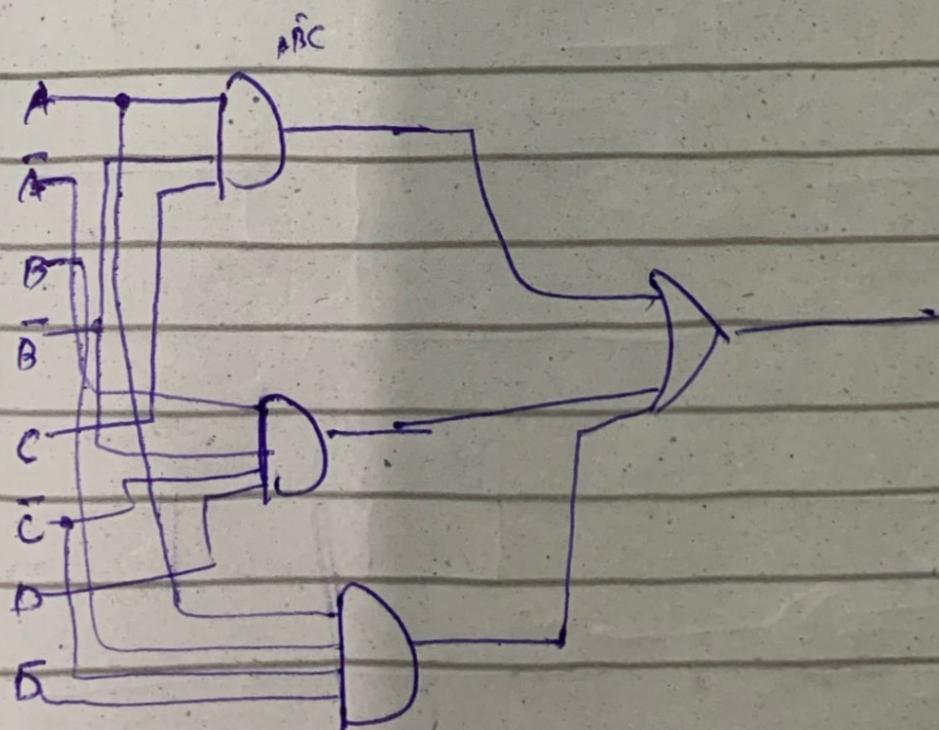


No. 1
Date _____
Page No. 1


Date _____

Question 3

Output:

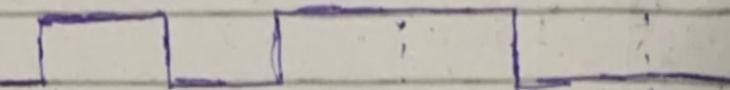


Q6) Active Low

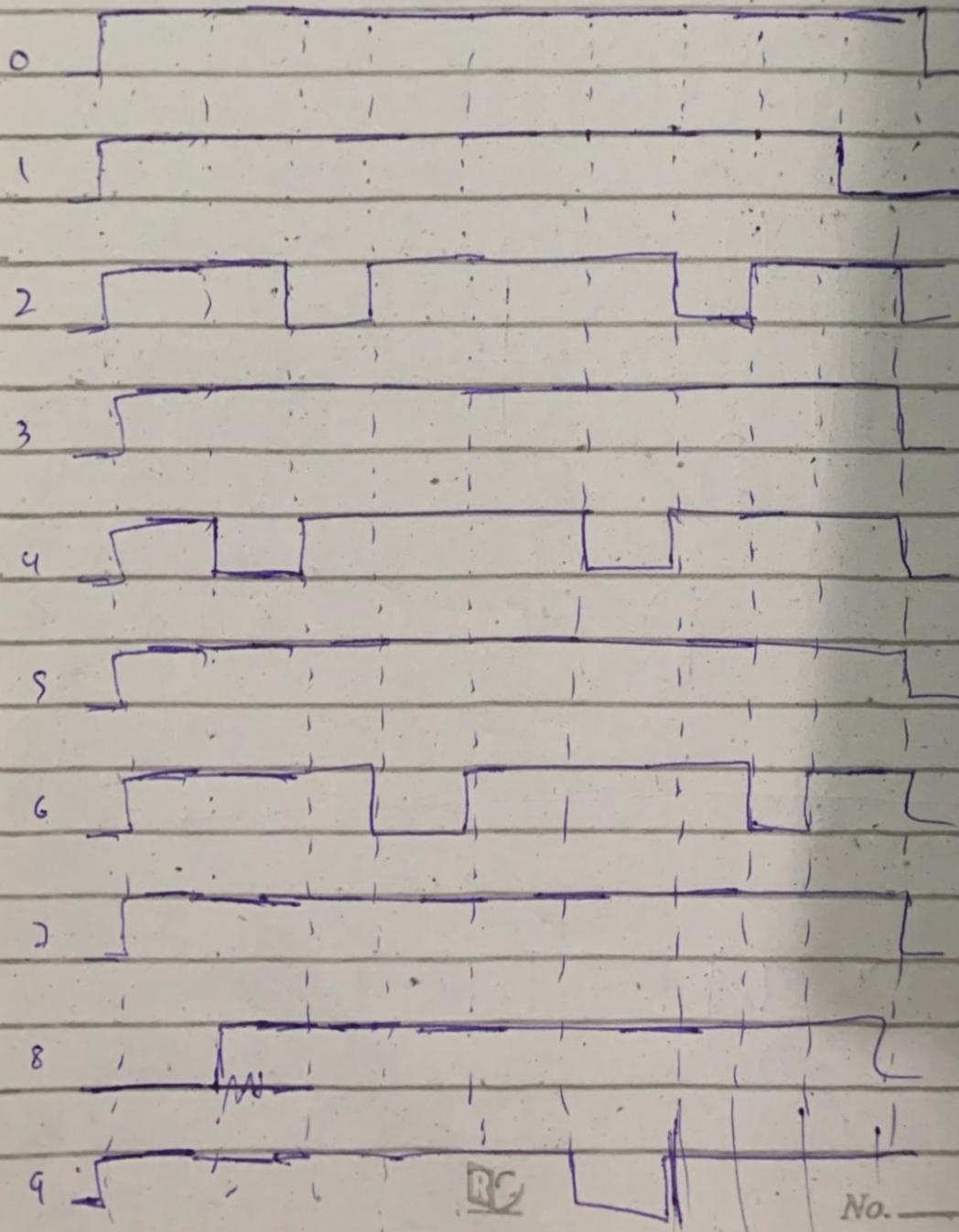


(a7)

- output is 1011 (which is 11 in decimal)
- It is not a valid BCD code

(a8)

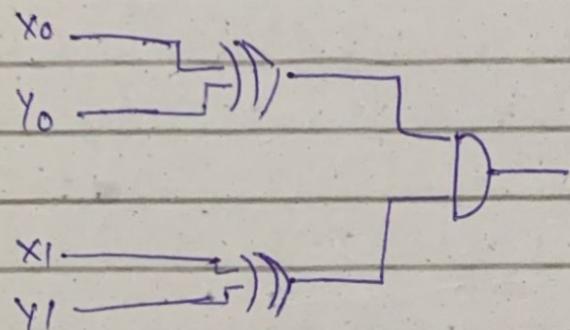

(a9)

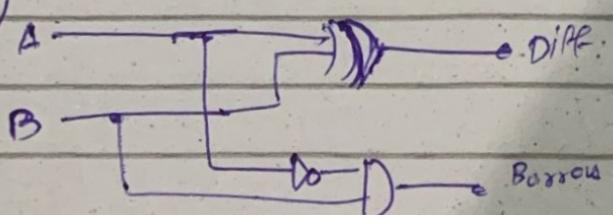

$$\text{Diff} = \bar{A}B + A\bar{B} = A \oplus B$$

$$\text{Borrow} = \bar{A}B$$

Date _____

(Q10)

A_2	A_1	B_2	B_1	$A > B$	$A = B$	$A < B$
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0



No. _____

$$\frac{(A \oplus B)}{(AB + A\bar{B})}$$

$$\frac{\bar{A}B + A\bar{B}}{(A+B) \cdot (\bar{A}+B)}$$

Date _____

For $A=B$

$$A_1 A_2 B_1 B_2 + A_1^{\bar{A}} A_2 B_1 B_2 + A_1 A_2^{\bar{B}} B_1 B_2 + A_1^{\bar{A}} B_1^{\bar{B}}$$

$$A_2 B_2 (A_1 B_1 + A_1^{\bar{B}} B_1) + A_2^{\bar{B}} B_2^{\bar{B}} (A_1 B_1 + A_1^{\bar{B}} B_1)$$


$$(A_1 B_1 + A_1^{\bar{B}} B_1) (A_2 B_2 + A_2^{\bar{B}} B_2)$$

$$\therefore \overline{A \oplus B} = AB + A\bar{B}$$

~~(A ⊕ B)~~

$$= (\overline{A_1 \oplus B_1}) \cdot (\overline{A_2 \oplus B_2})$$

For $A \neq B$

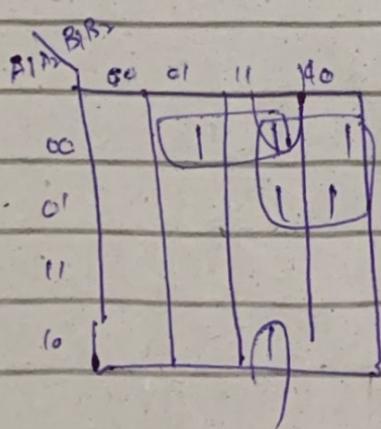

$$A_2 B_2 + A_2^{\bar{A}} A_1 B_1 + A_1^{\bar{A}} B_1 B_2$$


$$A_2^{\bar{A}} B_2 + A_1^{\bar{A}} B_1 (A_2 + B_2)$$

RF

No. _____

Date _____

A > B

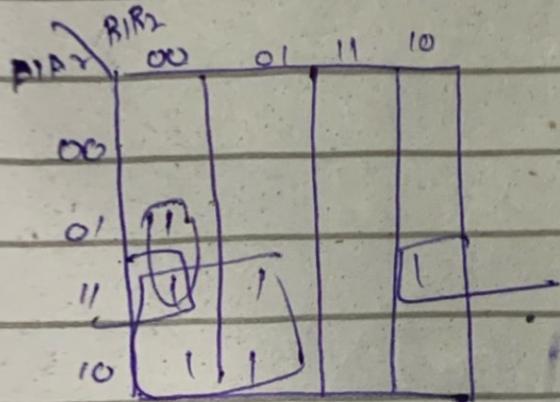

$$A_2 \bar{B}_2 + A_2 A_1 \bar{B}_1 + A_1 B_2 \bar{B}_1$$

$$A_2 \bar{B}_2 + A_1 \bar{B}_1 (A_2 + B_2)$$

Q.ii)

$$\begin{array}{ccc}
 : & S_1 & S_0 \\
 & 0 & 0 & D_6 \\
 & 0 & 1 & D_1 \\
 & 1 & 0 & D_2 \\
 & 1 & 1 & D_3
 \end{array}$$


a) $S_0 = 0 \quad S_1 = 1$
 output $\Rightarrow D_2 = 0$

b) $S_1 = 0 \quad S_0 = 1$
 output $\Rightarrow D_3 = 1$

c) $S_0 = 1 \quad S_1 = 0$
 output $\Rightarrow D_1 = 0$

Date _____

(in)

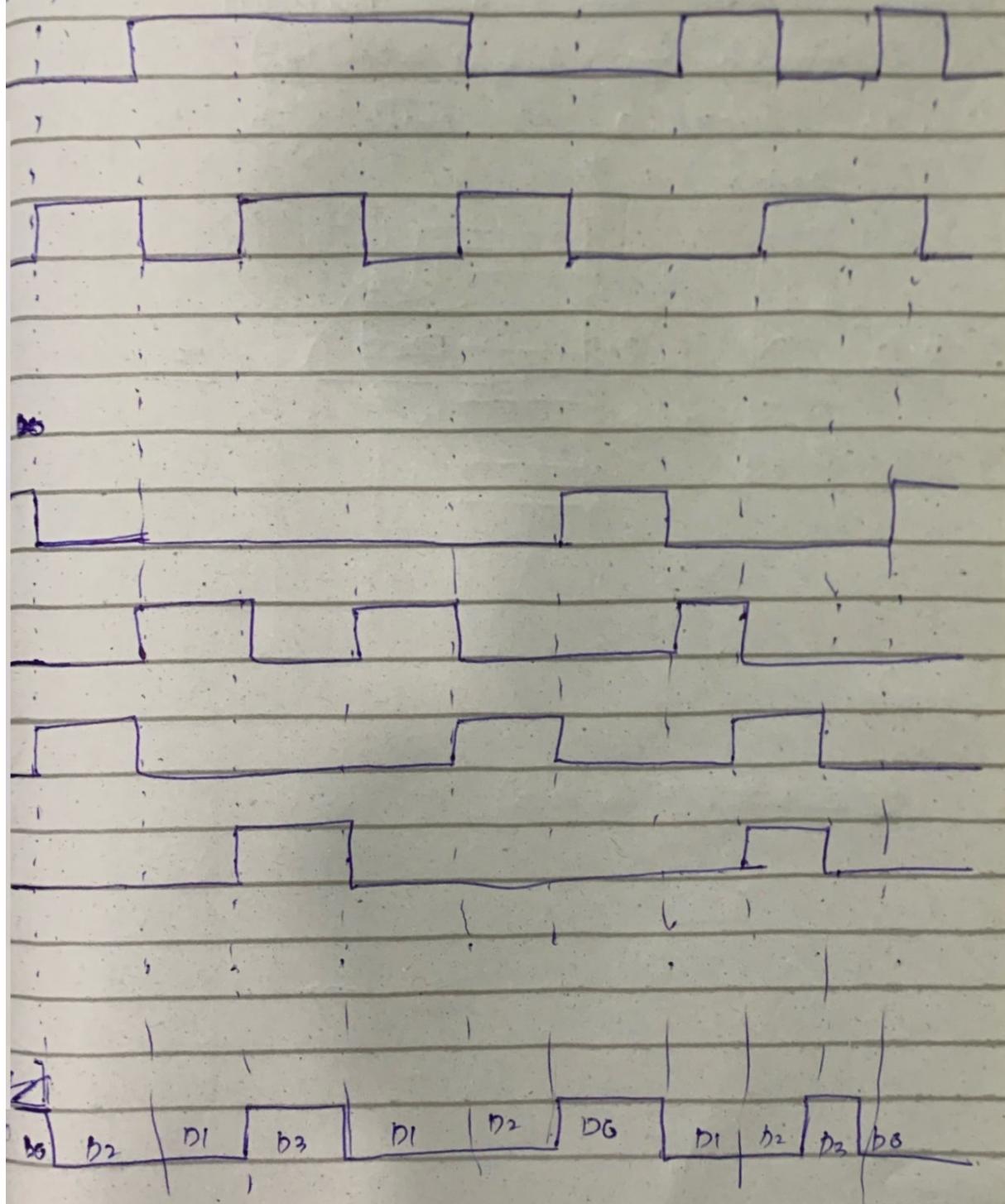


derived
from Problem

11

b1 b2 b3 b4 b5 b6 b7 b8
problem 3 selection bits were
unit No. 8


Date _____

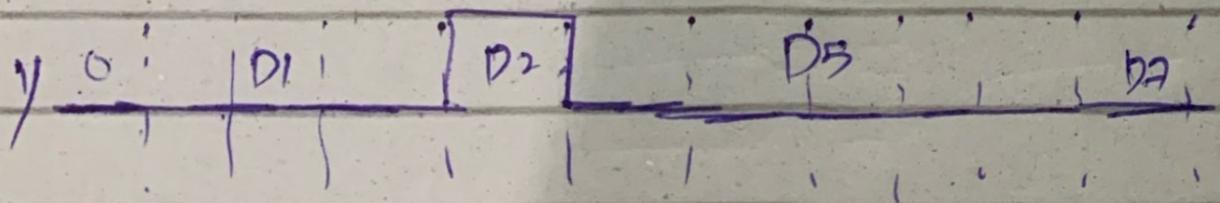(Q13) remember there is a bar on
Enabler \rightarrow means if $\overline{\text{enable}}$ is 1
then output = 0 if $\overline{\text{enable}}$ is 0 then
output is Y.



Q:14


0. 1 2 3 4 5 6 7 8 9 10 11 12 13 14

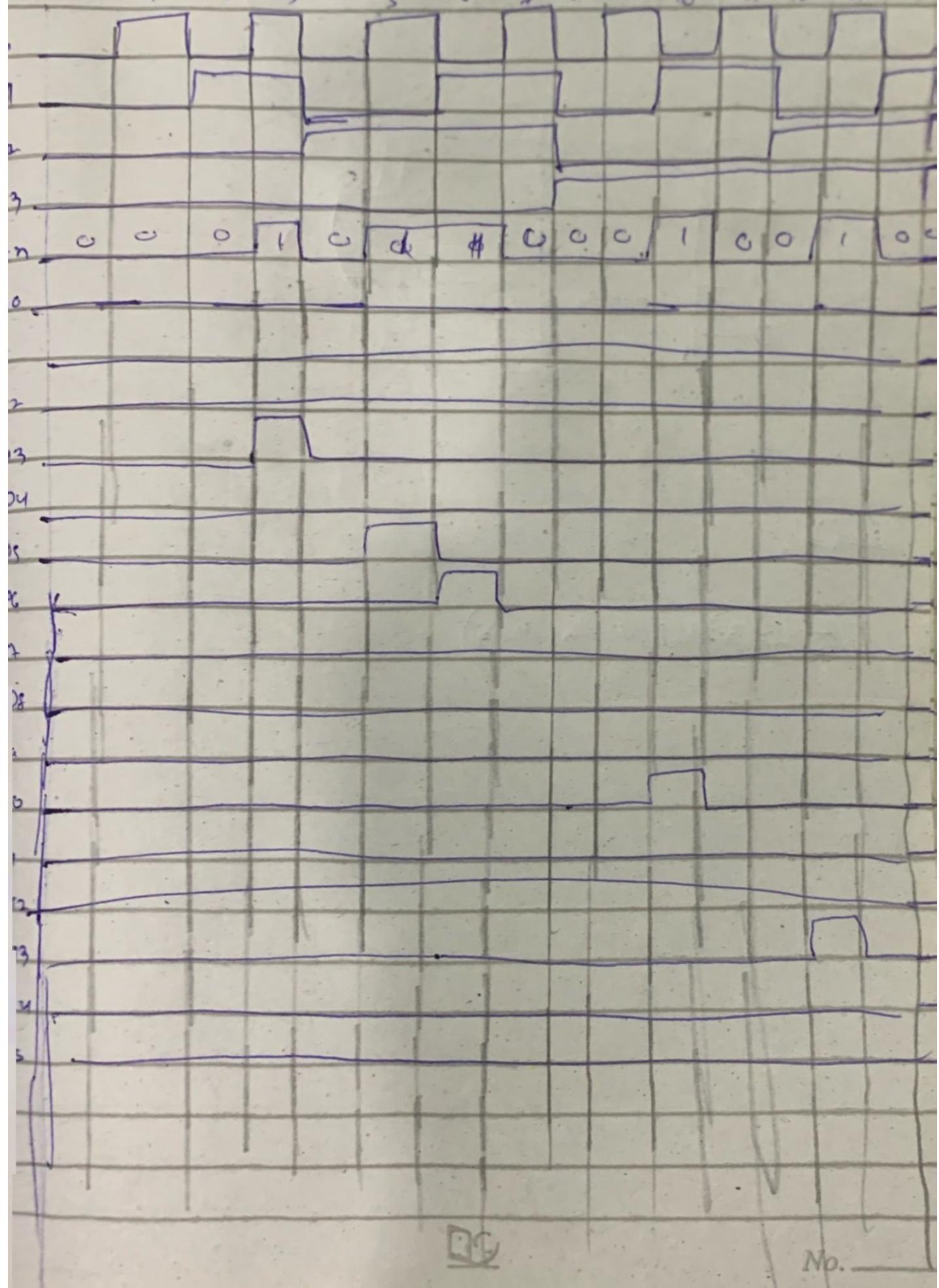

Date _____

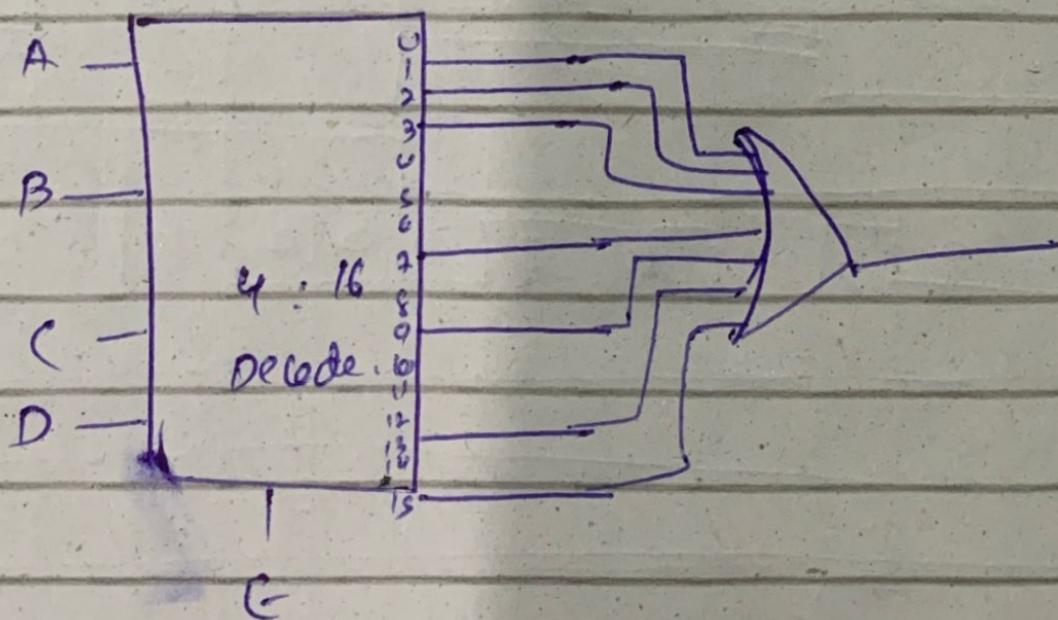Q: 15

$$F(A, B, C, D) = \sum (1, 2, 3, 7, 9, 13, 15)$$




4 : 16
decode.

~~$\sum (2, 3, 4, 8, 9, 10, 11, 15)$~~


Q1G $\in \{0, 3, 4, 8, 9, 10, 11, 15\}$

A_3	A_2	A_1	A_0	X	:	X
0	0	0	0	0	:	0
0	0	0	1	0	:	
0	0	1	0	1	:	1
0	0	1	1	1	:	
0	1	0	0	1	:	\bar{A}_0
0	1	0	1	0	:	
0	1	1	0	0	:	0
0	1	1	1	0	:	
1	0	0	0	1	:	1
1	0	0	1	1	:	
1	0	1	0	1	:	1
1	0	1	1	1	:	
1	1	0	0	0	:	0
1	1	0	1	0	:	
1	1	1	0	0	:	A_0
1	1	1	1	1	:	

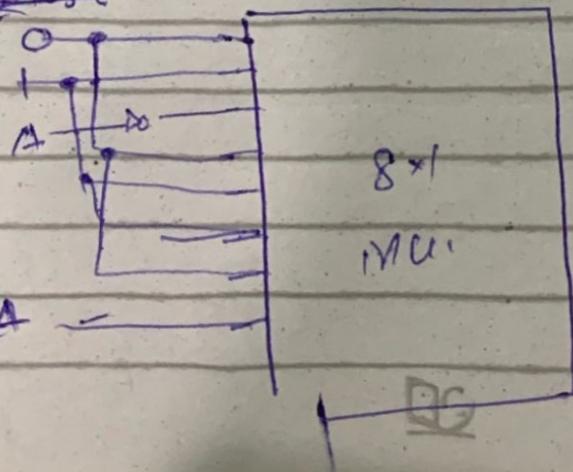~~4 logic~~


(2)

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

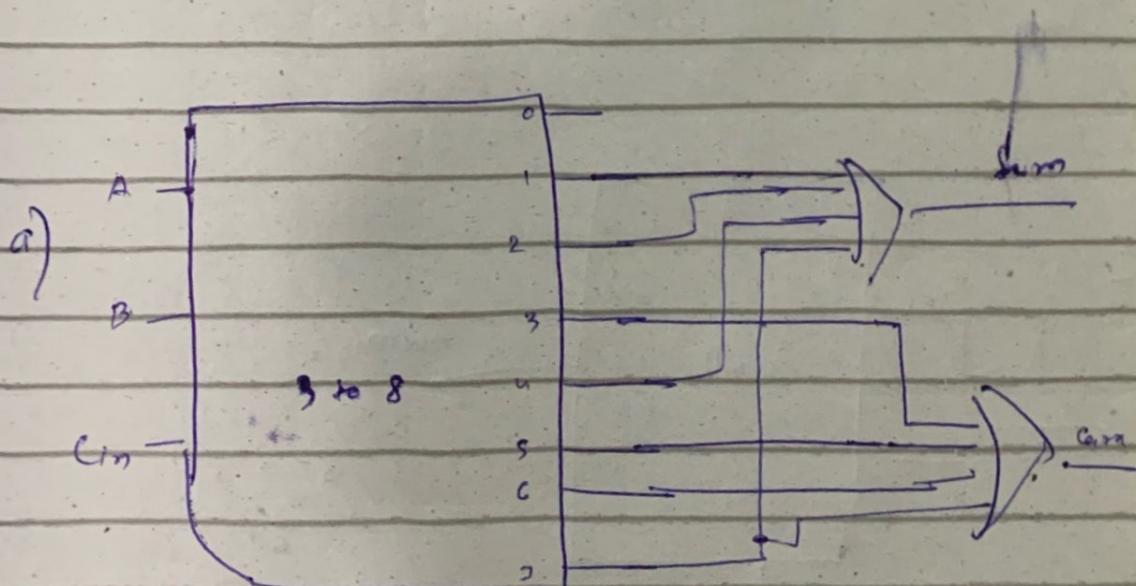


(b) 4×1


A	B	Cin	Sum's	Carry: C.
0	0	0	0 Cin	0 0
0	0	1	1	0
0	1	0	1	0
0	1	1	0 Cin	1 1
1	0	0	1 C	0
1	0	1	0	1
1	1	0	0 Cin	1 1
1	1	1	1	1 1

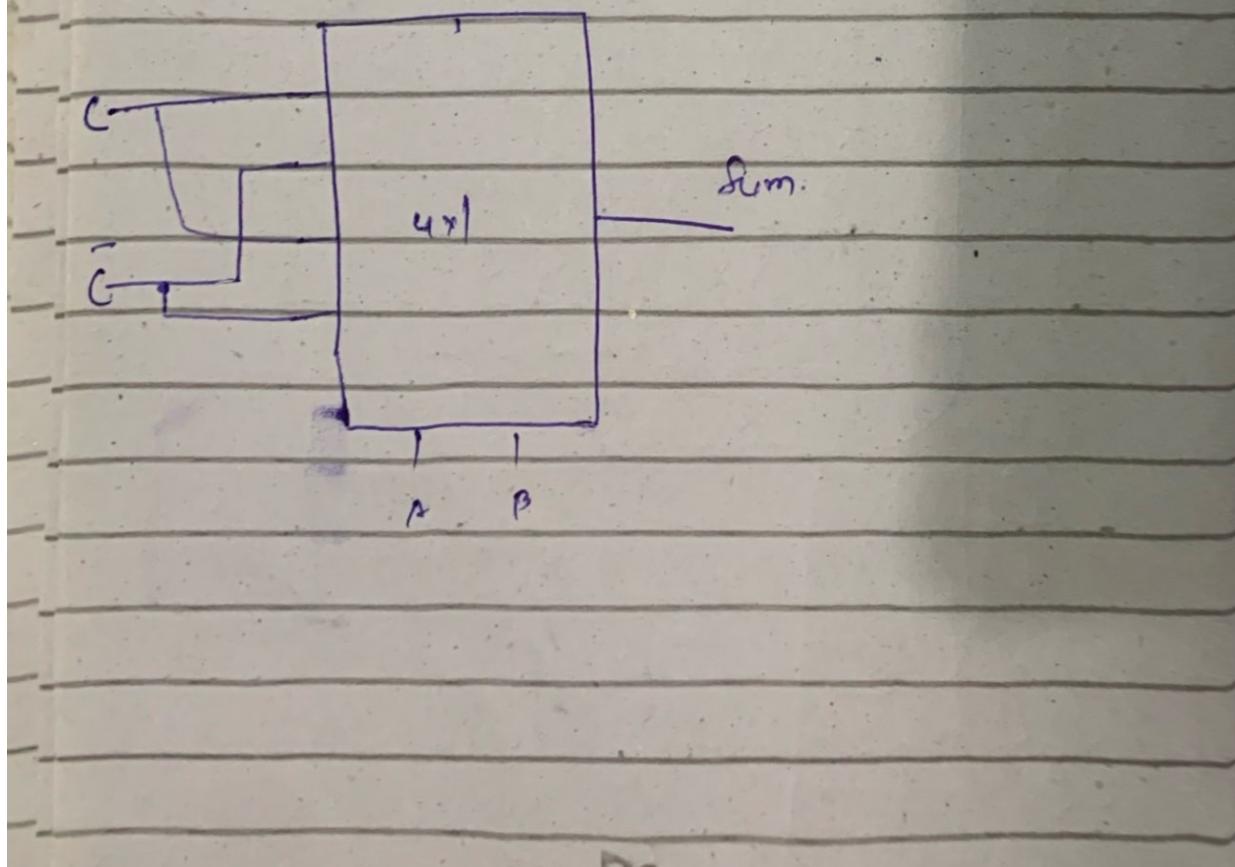+

Date _____

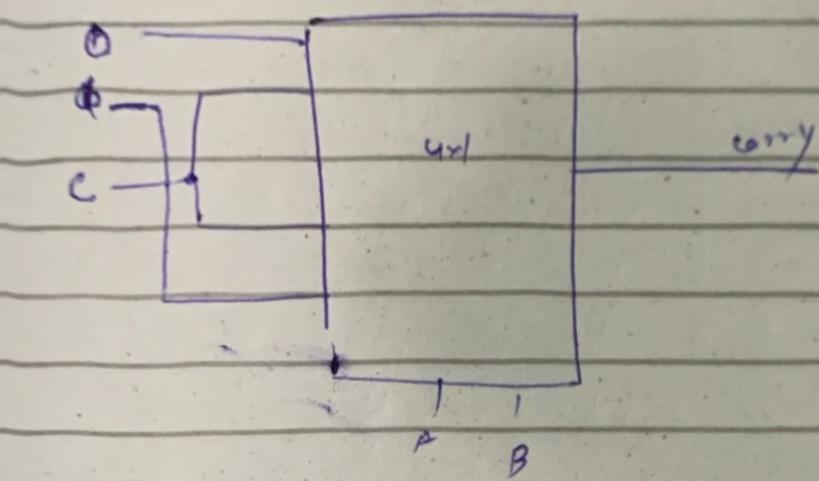

18

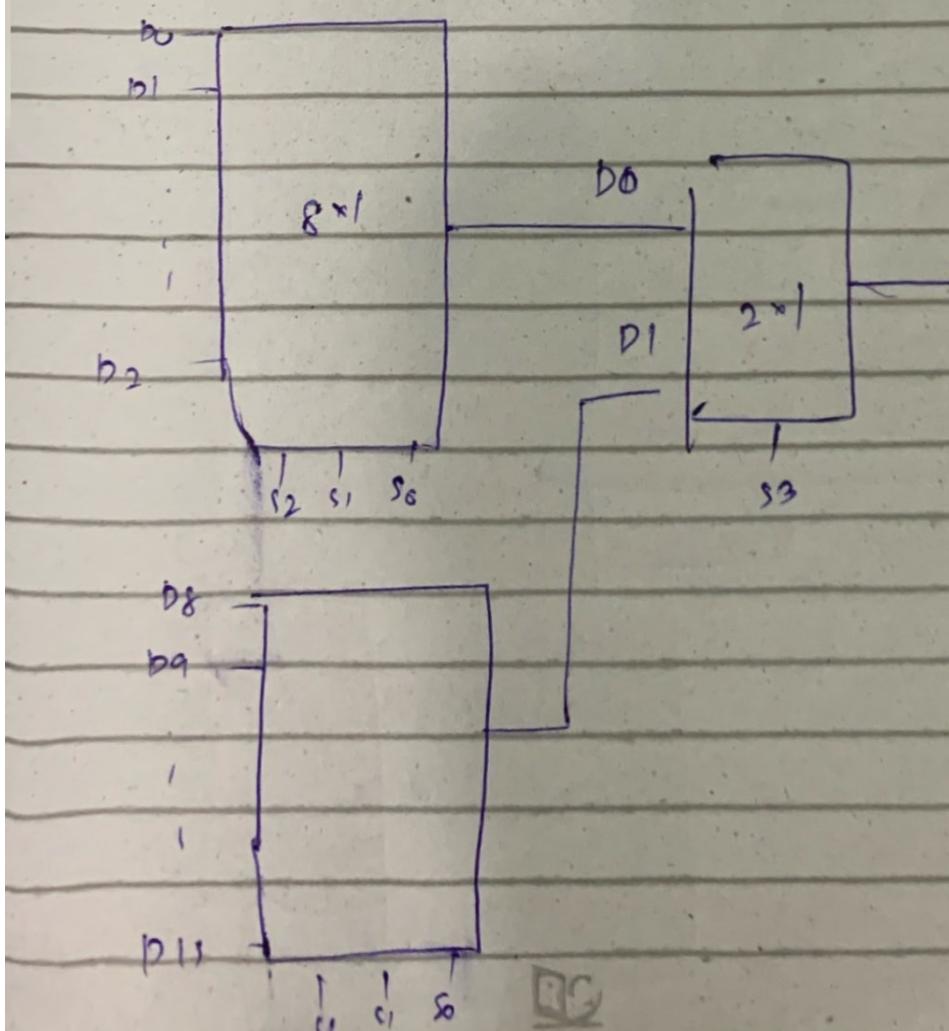

No. _____